



# North South University

## Department of Electrical & Computer Engineering

### Lab Report

Experiment No:	03
Experiment Title:	Universal Gates
Course Code:	CSE231L
Section:	17
Course Name:	Digital Logic Design Lab
Lab Group #:	02
Written By:	Md Mehrab Hossain Khandoker
Date of Experiment:	25/09/2024
Date of Submission:	02/10/2024
Due Date of Submission:	02/10/2024

Group Members ID:	Group Members Name:
2013278042	Tanjim Rayan
2231047642	Tanvir Ahmed
2311511042	Md Mehrab Hossain Khandoker
2311776642	Nafsin Nasama Salmee
2311712642	Walidur Rahman

# Objectives

- Get introduced to the concepts of Universal Gates
- Simulating basic logic gates and boolean functions using universal gates and verifying using their respective truth tables.


## Equipment List

- Trainer Board
- 2 x IC 7400 Quadruple 2-input NAND gates
- 2 x IC 7402 Quadruple 2-input NOR gates
 
## Theory


Universal Gates are defined as those gates that can be used to replicate the boolean operation of all the logic gates, using the gate itself only. Of all the available logic gates, only the NAND and NOR gates are found to be the Universal Gates. Therefore, with the use of only NAND or NOR gates, logic gates such as AND, OR, NOT, XNOR, XOR can be constructed.

NAND gate: A NAND gate accepts two inputs A and B, performing AND operation on them ( $AB$ ) and the output is delivered by inverting ( $AB$ );  $\overline{AB}$ .




NAND gate

 NOR gate: A NOR gate accepts two inputs A and B, performing OR operation on them ( $A + B$ ) and the output is delivered by inverting ( $A + B$ );  $\overline{A + B}$



NOR Gate

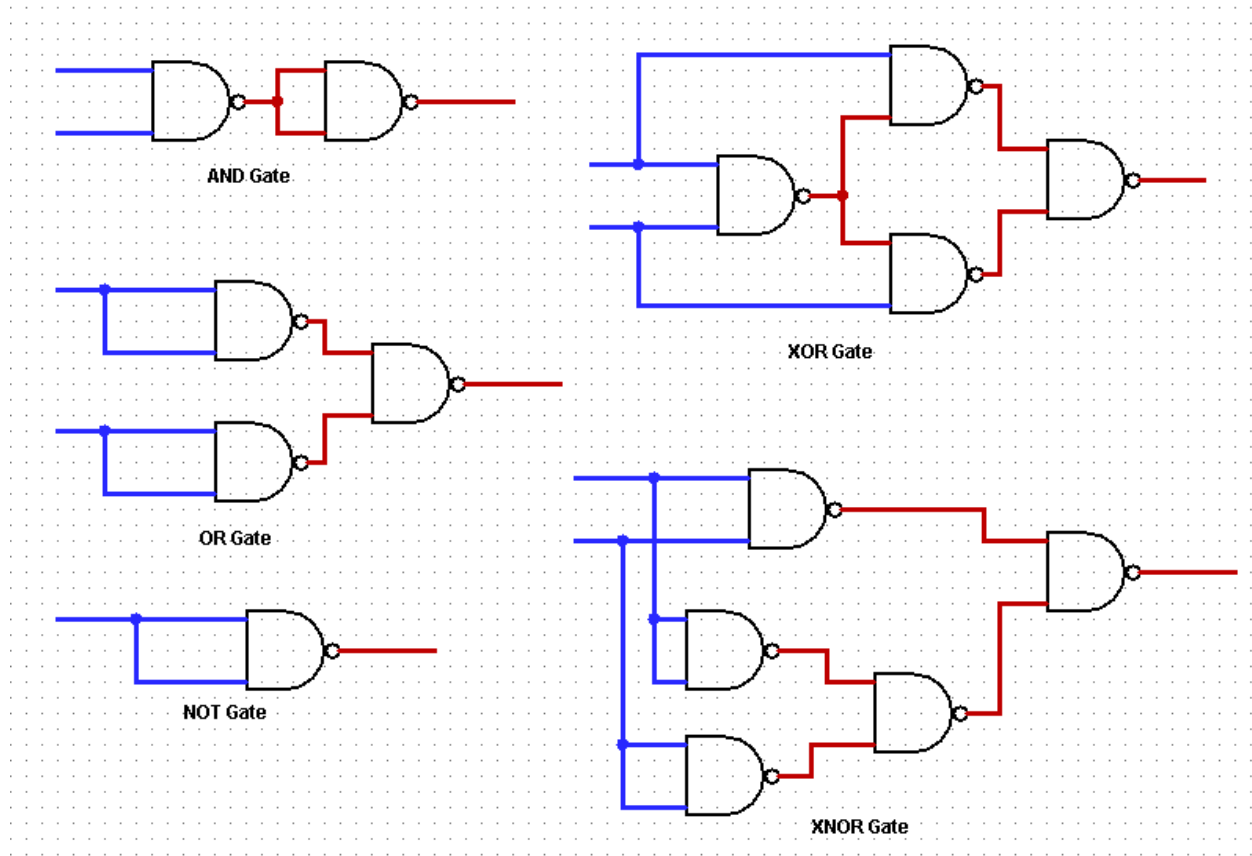

Logic Gates using NAND Gate

## Circuit Diagram:



 
 


Figure D1: Implementation of XOR and XNOR using NAND gates

 

NOT

 

OR

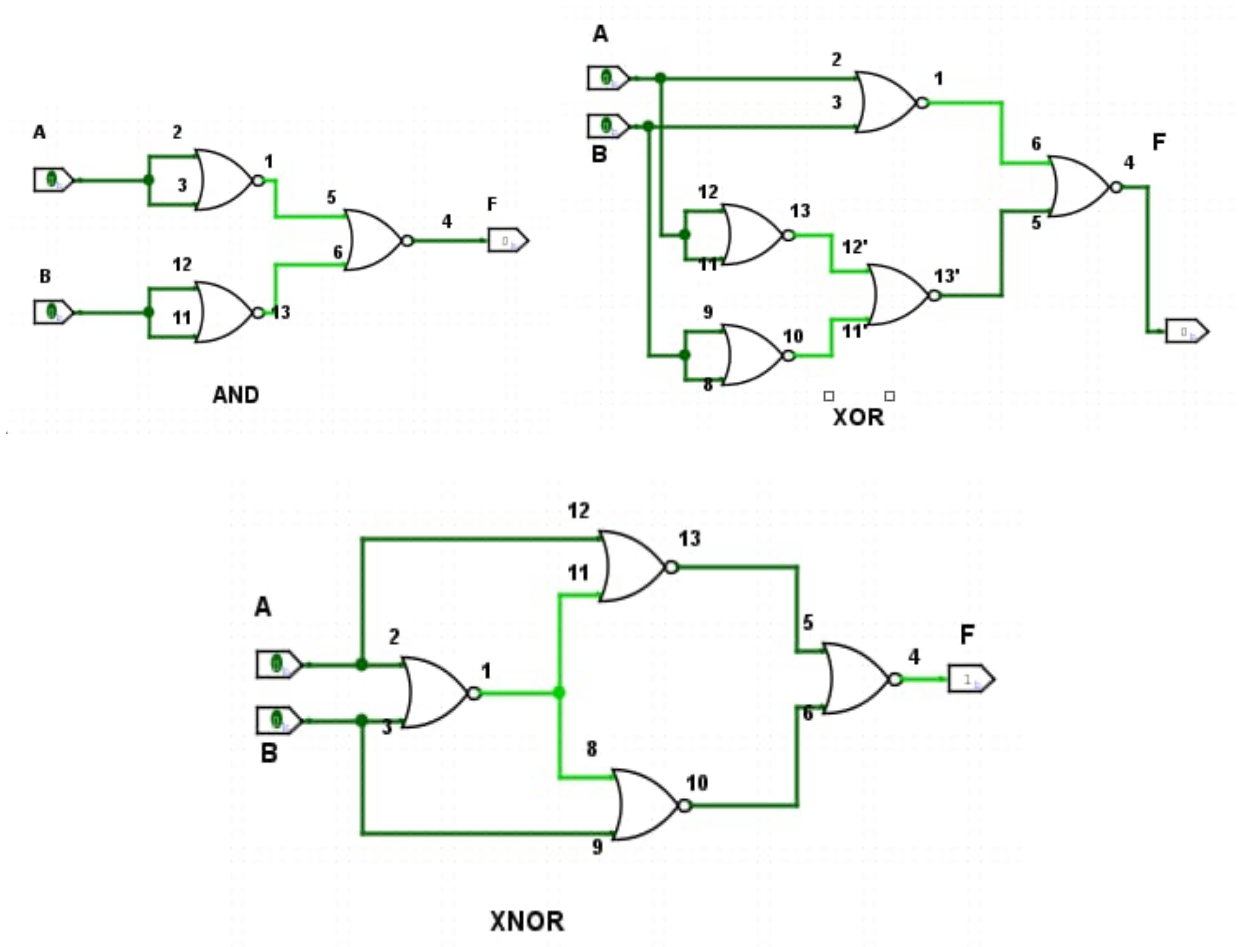


Figure D2: Implementation of NOT, AND, OR, XOR and XNOR using NOR gates.

## Data Table & Equation

$A B C$	$I_1 = A C$	$I_2 = B \bar{C}$	$F = I_1 + I_2$
0 0 0	0	0	0
0 0 1	0	0	0
0 1 0	0	1	1
0 1 1	0	0	0
1 0 0	0	0	0
1 0 1	1	0	1
1 1 0	0	1	1
1 1 1	1	0	1

Table D1: Truth table of combinational circuit in Figure B2

## Minterms and Maxterms

Input Reference	A B C	F	Max term
0	0 0 0	0	$A + B + C$
1	0 0 1	0	$A + B + \bar{C}$
2	0 1 0	1	$A + \bar{B} + C$
3	0 1 1	0	$A + \bar{B} + \bar{C}$
4	1 0 0	0	$\bar{A} + B + C$
5	1 0 1	1	$\bar{A} + B + \bar{C}$
6	1 1 0	1	$\bar{A} + \bar{B} + C$
7	1 1 1	1	$\bar{A} + \bar{B} + \bar{C}$

<b>2<sup>nd</sup> Canonical Form</b>	$F = \Pi(0,1,3,4)$	$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + C)$
--------------------------------------	--------------------	--

## Minimization

$$\therefore F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + C)$$

$$\therefore (A + B + C)(A + B + \bar{C})$$

$$= A + B$$

$$\therefore (A + \bar{B} + \bar{C})(\bar{A} + B + C)$$

$$= B\bar{C} + \bar{A}\bar{B} + AC$$

$$\therefore F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + C)$$

$$\Rightarrow F = (A + B)(B\bar{C} + \bar{A}\bar{B} + AC)$$

$$\Rightarrow F = AB\bar{C} + A\bar{A}\bar{B} + AAC + BB\bar{C} + \bar{A}\bar{B}B + ABC$$

$$\Rightarrow F = AB\bar{C} + AC + B\bar{C} + ABC$$

$$\Rightarrow F = AC + B\bar{C}$$

## Discussion


The objective behind performing this experiment was to understand the functionality and importance of universal gates (NAND and NOR) in constructing any logic circuit. We have learned how universal gates can be used to implement all the basic logic gates (NOT, AND, OR) as well as Exclusive gates (XOR, XNOR). The circuits were implemented using these gates and verified through truth tables.

At first, we implemented all the basic logic gates and exclusive gates using only the NAND gates. Then, the process was repeated using the NOR gates. After this, a combinational circuit was constructed that consists of several basic logic gates, using NAND gates. By observing the output, we found that our NAND-only combinational circuit successfully replicated the output without compromising any functionality. We further confirmed this equivalence using the truth table and simulating the circuit on Logisim. The experimental results aligned with the expected values and simulated results, demonstrating that the universal gates can indeed replicate the functions of other gates.


In conclusion, this experiment reinforced the concept of universal gates that these gates are capable of constructing any other logic gate or combinational circuits. No significant problems were encountered while performing the experiment. However, careful pin mapping and circuit design were crucial to ensure correct connections and outputs. Proper verification using truth tables helped in identifying and rectifying any minor wiring issues.

## Simulation:

Simulation of the logic circuit in Fig B.2 using only NAND gates for the input  $ABC = 000$

 

**Figure D3: Universal(NAND) gate implementation of the circuit of figure B2**

 

Simulation of the logic circuit in Fig B.2 using only NOR gates for the input  $ABC = 000$



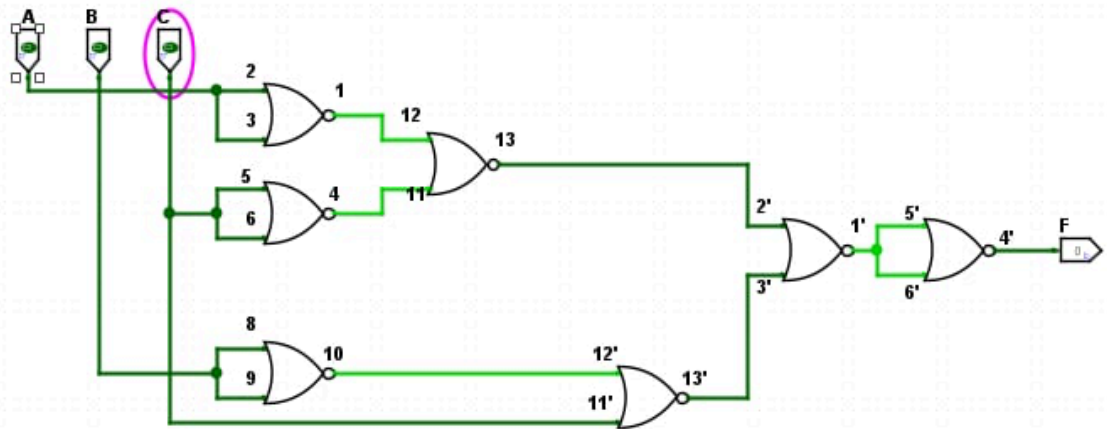


Figure D3: Universal(NOR) gate implementation of the circuit of figure B2

